

Content

- ▶ Review of Last Lecture.
- ▶ Transfer Function.
- ▶ Transfer function of RC and RLC electrical circuit.
- ▶ Examples of Transfer function
- ▶ Order of System & its type


▶

Learning Objectives

- ▶ Able to define use of TF in control system.
- ▶ Able to derive expression for open loop and closed loop system.
- ▶ Transfer function of RC and RLC electrical circuits.

Transfer Function

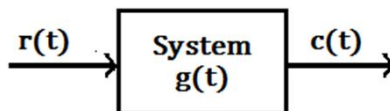- ▶ Ratio of Laplace transform of *output (or response)* to Laplace transform of *input (or excitation)* under the assumption of zero initial conditions is defined as the transfer function of given system.



$c(t)$ – output

$$L\{c(t)\} = C(s)$$

Therefore,

$r(t)$ – input

$$L\{r(t)\} = R(s)$$

$$G(s) = C(s) / R(s)$$

$g(t)$ – system function

$$L\{g(t)\} = G(s)$$

Properties of Transfer Function

- ▶ TF is defined only for linear time invariant systems. it is not defined for non-linear systems.
- ▶ Transfer function is independent of inputs to system.
- ▶ Systems poles/zeros can be found out from Transfer function.
- ▶ Once TF is known, any output for any given input, can be known.
- ▶ System differential equation can be obtained by replacement of variable 's' by 'd/dt'.



Laplace Transform of Electrical N/W


Element	Time-Domain	S-Domain
R	$i(t) * R$	$I(s) * R$
L	$L . di(t)/dt$	$Ls * I(s)$
C	$1/C . \int i(t)dt$	$1/sC * I(s)$

R- Resistance
L- Inductance

C-Capacitance
I- Current



Transfer Function of Closed Loop System

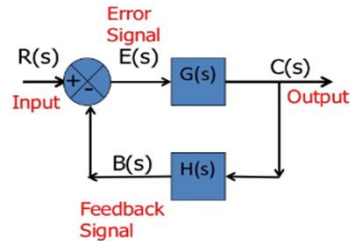

Error signal is given by,

$$E(s) = R(s) - B(s) \text{ -----(1)}$$

Thus,

$$R(s) = E(s) + B(s)$$

Gain of feedback n/w is given by,

$$H(s) = B(s)/C(s)$$

Thus,

$$B(s) = H(s).C(s) \text{ -----(2)}$$

Gain for CL system is given by,

$$G(s) = C(s)/E(s)$$

$$\text{Thus, } C(s) = G(s).E(s) \text{ -----(3)}$$

Substitute the value of E(s) from Eq. 1 to 3

$$C(s) = G(s).[R(s) - B(s)]$$

Thus,

$$C(s) = G(s).R(s) - G(s).B(s) \text{ -----(4)}$$

Substitute the value of B(s) from Eq. 2 to 4

$$C(s) = G(s).R(s) - G(s).H(s).C(s)$$

$$G(s).R(s) = C(s) + G(s).H(s).C(s)$$

$$G(s).R(s) = C(s)[1 + G(s).H(s)]$$

Transfer function is given by,

$$\text{T.F.} = C(s)/R(s) = G(s)/1 + G(s).H(s)$$



Laplace Transform of ' R '

- ▶ Resistor are time and frequency invariant. Therefore, transform of a resistor is same as the resistance of resistor.

$$L\{\text{Resistor}\} = R(s)$$



Laplace Transform of ' C '

- ▶ Let us look at relationship between voltage, current and capacitance in time domain.

$$i(t) = C \frac{dv(t)}{dt}$$

- ▶ Solving for voltage, we get the following integral;

$$v(t) = \frac{1}{C} \int_{t_0}^{\infty} i(t) dt$$

- ▶ Then transforming this equation into Laplace domain, we get the following;

$$V(s) = \frac{1}{C} \frac{1}{s} I(s)$$

- ▶ Again, solving for ratio $V(s)/I(s)$, we get the following;

$$\frac{V(s)}{I(s)} = \frac{1}{sC}$$

- ▶ Therefore, transform for a capacitor with capacitance C is given by,

$$L\{\text{capacitor}\} = \frac{1}{sC}$$



Laplace Transform of ' L '

- ▶ Let us look at relationship between voltage, current and inductance in time domain.

$$v(t) = L \frac{di(t)}{dt}$$

- ▶ Then transforming above equation into Laplace domain, we get the following;

$$V(s) = sLI(s)$$

- ▶ Again, solving for ratio $V(s)/I(s)$, we get the following;


$$\frac{V(s)}{I(s)} = sL$$

- ▶ Therefore, transform for an inductance with inductance L is given by,

$$L\{\text{inductor}\} = sL$$



Transfer Function of RC Network

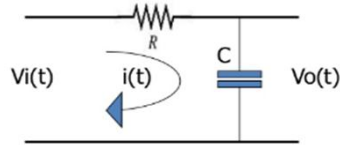

- ▶ Apply KVL for input loop,

$$v_i(t) = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$$

- ▶ Taking Laplace transform of above equation, we get;

$$V_i(s) = RI(s) + \frac{1}{sC} I(s) \text{-----(1)}$$

- ▶ Apply KVL for output loop,

$$v_o(t) = \frac{1}{C} \int_0^t i(t) dt$$

- ▶ Taking Laplace transform of above equation, we get;

$$V_o(s) = \frac{1}{sC} I(s) \text{-----(2)}$$

$$\therefore I(s) = sC \cdot V_o(s) \text{-----(3)}$$

- ▶ From equation 1,

$$V_i(s) = I(s) \left(R + \frac{1}{sC} \right) \text{-----(4)}$$

- ▶ From equation 3 & 4,


$$V_i(s) = V_o(s) \cdot sC \cdot \left(R + \frac{1}{sC} \right) \text{-----}$$

Transfer Function of RC Network


$$\text{Transfer Function} = G(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{sC \cdot \left(R + \frac{1}{sC} \right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{sC \cdot \left(\frac{sCR + 1}{sC} \right)}$$

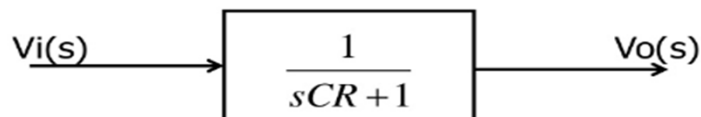
$$\frac{V_o(s)}{V_i(s)} = \frac{1}{sCR + 1}$$



Transfer Function of RLC Network

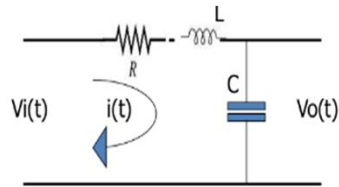

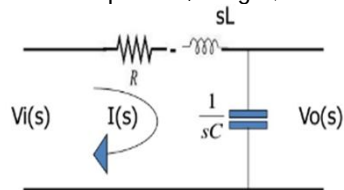- ▶ Taking Laplace transform of above equation, we get;



- ▶ Apply KVL for input loop,

$$Vi(s) = RI(s) + sLI(s) + \frac{1}{sC}I(s)$$

$$\therefore Vi(s) = [R + sL + \frac{1}{sC}]I(s) \text{-----(1)}$$

- ▶ Apply KVL for output loop,

$$Vo(s) = \frac{1}{sC}I(s) \text{-----(2)}$$

Transfer Function of RLC Network

From equation 1 & 2,


$$\text{Transfer Function} = \frac{Vo(s)}{Vi(s)} = \frac{\frac{1}{sC} \cancel{I(s)}}{[R + sL + \frac{1}{sC}] \cancel{I(s)}}$$

$$= \frac{1}{sC} \frac{1}{[R + sL + \frac{1}{sC}]}$$

$$= \frac{\frac{1}{sC}}{\frac{sCR + s^2LC + 1}{sC}}$$

$$= \frac{1}{sCR + s^2LC + 1}$$

$$= \frac{1}{s^2LC + sCR + 1}$$

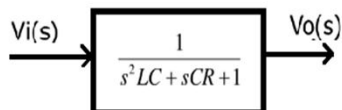

Order of System

- ▶ Order of control system is defined as the highest power of s present in denominator of closed loop transfer function $G(s)$ of unity feedback system.
- ▶ A **proper system** is a system where the degree of denominator is larger than or equal to the degree of numerator polynomial.

$$G(s) = \frac{s+1}{(s^2+2s+1)}$$



Order of System

Q. Define the order of given system

$$G(s) = \frac{(S+1)}{S^2+2S+1}$$

Answer: The highest power of equation in denominator of given transfer function is '2'. Hence, the order of given system is two.



Find the order of given system

$$G(s) = \frac{S(S+2)}{S(S+2)(S+1)}$$

Solution: To obtain highest power of denominator ,
Simplify denominator polynomial.

$$S(S+2)(S+1)=0$$

$$S(S^2+3S+2)=0$$

$$S^3+3S^2+2S=0$$

The highest power of equation in denominator of given transfer function is '3'. Hence, given system is 'Third Order System'

The degree of denominator is larger than the numerator. Hence, system is 'Proper System'



Types of System


▶ Depending on highest power of denominator,
system are classified as:

- ▶ Zero Order System
- ▶ First Order System
- ▶ Second Order System



Zero Order System

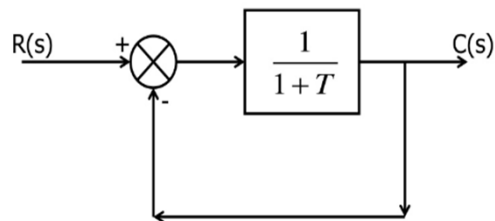- ▶ If highest power of complex variable 's' present in characteristic equation is zero, then it is called as **"Zero Order System"**



Zero Order System

- ▶ Consider a unity feedback system with transfer function

$$G(s) = \frac{1}{1+T}$$

Hence, characteristic equation is given by ,

$$1 + T = 0$$

or

$$1 + s^0 T = 0$$


Here, highest power of s is equal to 0,

Hence, system given above is Zero Order System.

Practical Example: Amplifier type control system.

First Order System

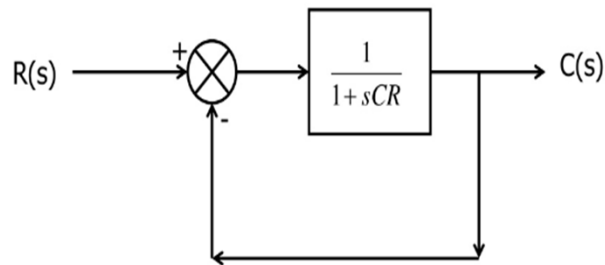- ▶ If highest power of complex variable 's' present in characteristic equation is one, then it is called as **"First Order System"**



First Order System

- ▶ Consider a unity feedback system with transfer function

$$G(s) = \frac{1}{1+sCR}$$

Hence, characteristic equation is given by ,

$$1 + sCR = 0$$


Here, highest power of s is equal to 1,

Hence, system given above is First order system

Practical Example: RC circuits, thermal type systems .

Second Order System

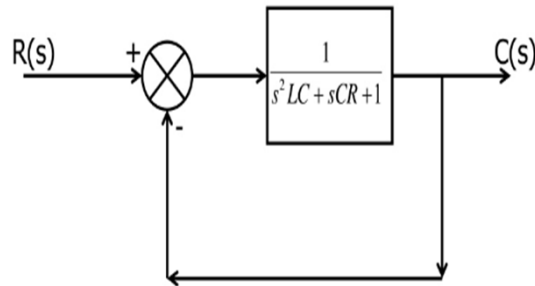- ▶ If highest power of complex variable 's' present in characteristic equation is two, then it is called as **"Second Order System"**



Second Order System

- ▶ Consider a unity feedback system with transfer function

$$G(s) = \frac{1}{s^2 LC + sCR + 1}$$

Hence, characteristic equation is given by ,

$$s^2 LC + sCR + 1 = 0$$

Here, highest power of s is equal to 2,

Hence, system given above is First order system

Practical Example: RLC circuits, Robotic control systems .

Summary

- ▶ Transfer Function.
 - ▶ Transfer Function of RC and RLC circuits.
 - ▶ Order of system.
 - ▶ Types of system.
-

